

# ME 103 Discussion 1

Week of 1/19

# Syllabus Review - Contact Information

## Course staff

Name	E-mail	Office hours
<b>Dr. George Anwar</b> Course instructor	<a href="mailto:ganwar@berkeley.edu">ganwar@berkeley.edu</a>	Monday, Wednesday, Friday 10:00 AM – 12:00 PM, Hesse 50B
<b>Steph Akakabota</b> (they/ them) GSI	<a href="mailto:sakakabota@berkeley.edu">sakakabota@berkeley.edu</a>	Tuesdays 1:00 - 2:00 PM, Hesse 50B + <i>Thursdays 1-2 PM</i>
<b>Larry Hui</b> GSI	<a href="mailto:larryhui7@berkeley.edu">larryhui7@berkeley.edu</a>	Wednesday 12:00 - 2:00 PM, Hesse 50B, or by request!
<b>Dalil Ashong</b> Tutor	<a href="mailto:dalilashong@berkeley.edu">dalilashong@berkeley.edu</a>	Friday 9:00 - 10:00 AM, Hesse Fishbowl (subject to change)
<b>Alyn Panggabean</b> Tutor	<a href="mailto:alyn@berkeley.edu">alyn@berkeley.edu</a>	N/A

## Class Website :)


- This semester, we are also going to have a course website in an effort to help keep the course more organized.
- All lecture recordings, lecture pdfs, discussion recordings, notes, textbook, homework, OH schedule, syllabus, important lab and project details will be found there!
- Please email any TA if you have questions or suggestions. Link: [ucb-me103.github.io/me103-sp26site](https://ucb-me103.github.io/me103-sp26site)
  - bookmark it!

# Syllabus Review - Lab Structure

- Labs will begin next week in Hesse 122, please bring your Microkit!
- Groups of 3-4 students (some exceptions can be made)
- At least 1 Microkit per group
- Labs will be due by the minute before your next lab.
  - i.e. Tuesday 2-5pm's lab is due the following week at 1:59 pm.
- If you have any questions during lab, we will also be trying [bearqueue](#)<sup>1</sup>.

<sup>1</sup> Thanks Elliot! Hopefully, it will be ready by next week!



# Note about LaTeX

- All assignments you are handing in for ME103 should be typeset in LaTeX. We recommend that you
  - use Overleaf, an online LaTeX editor!
  - edit locally using TeX Editor or VSCode
- You **DO NOT** need to draw diagrams using Tikz (this would be unnecessarily cruel...) However, if you are going into academia, it might be helpful to learn how. <https://tikzmaker.com/editor> is a great tool to get started! 
- Ask Larry for any LaTeX help.
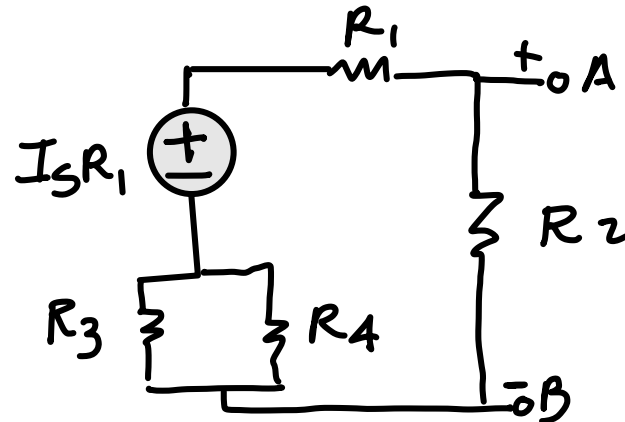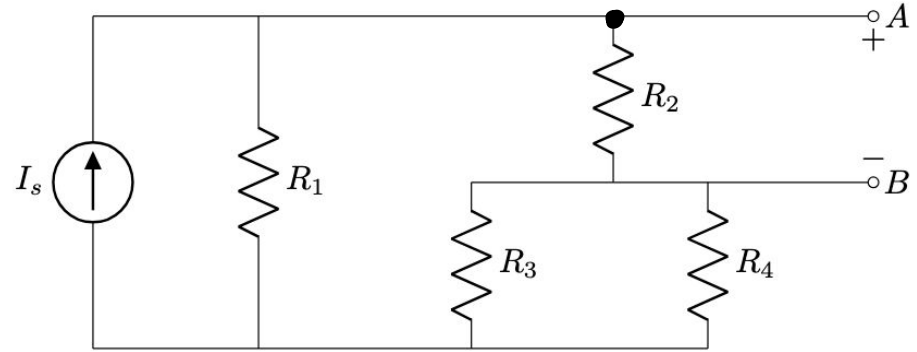
# Thévenin/Norton Equivalent Circuits

$$V_{th}I_s = P_{th}$$

- Replace current and  $R_1$  with voltage source  $I_s R_1$  in series with  $R_1$ .
- $V_{th}$  is V at node a, or Voltage through  $R_2$ , voltage divider eq
- Short voltage source and find equivalent resistance to find  $R_{th}$ .




# Zener Diodes as Voltage Regulators

- Uses:
  - To vary or regulate the output voltage
  - $R_s$  varies to regulate the current through the diode.
  - Turns off if  $V_z$  gets below its specific (breakdown) voltage (i.e. current too high, resistance too low)

• Zener C9V4 =  $9.4\text{ V} = V_z$

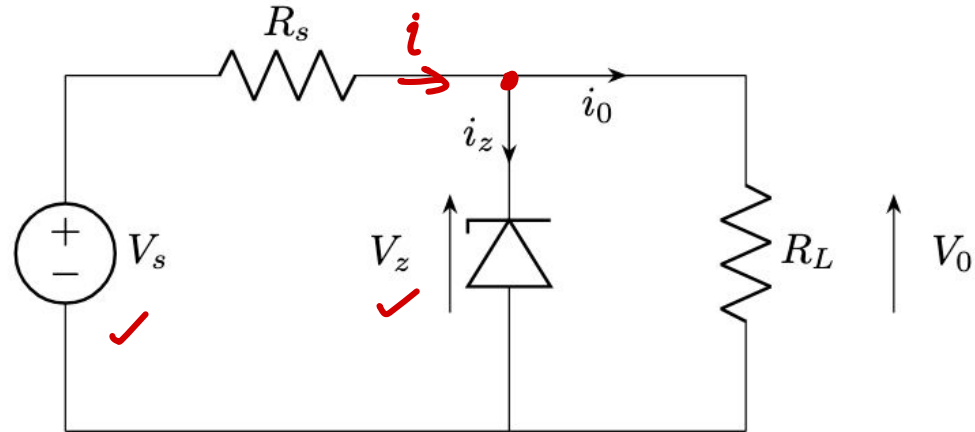- Junction Math =  $i_z = (V_s - V_z)/R_s - i_0$
- When load is disconnected,  $i_0 = 0$
- $P = IV \rightarrow$  get  $i_z \rightarrow$  solve for  $R_s$



# Zener Diodes as Voltage Regulators

- Current over the load ( $i_o$ ) cannot exceed maximum current for diode =  $i_{z,max} = 7.5/9.4 = 0.8$  A. Check if the resistances are high enough to ensure that the diode stays ON.
- If the diode is OFF, no current goes through that path → Simple voltage divider
  - $P = V_o^2/R_L$  ←
- Diode is on for current below 0.8 A → Voltage stays at 9.4V

$$P = \frac{9.4V^2}{50\Omega}$$


$$P = \frac{9.4V^2}{100\Omega}$$

$$\frac{9.4}{10} = 0.94A$$

10Ω 50Ω 100Ω

$$P = IV$$


$$\frac{7.5W}{9.4} = 0.8A$$

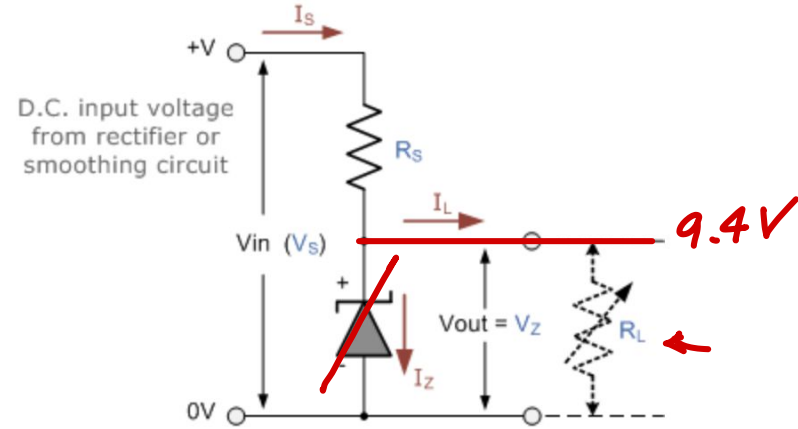


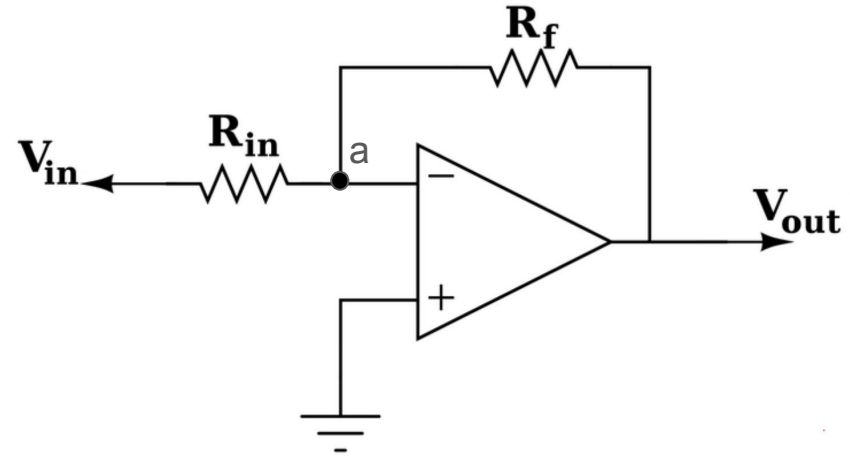
# Inverted Op Amp

- Golden Rules:
  - $V_- = V_+$
  - $i_- = i_+ = 0$
- Perform nodal analysis at a
- DC Gain =  $-R_f/R_{in}$




# Active Op Amp (inverting)

$$\frac{V_o^2}{R_1} = \frac{V_{in}^2}{2R_2} \quad \frac{V_o^2}{V_{in}^2} = \frac{1}{2}$$

- $P = V^2/R$   $\leftarrow$
- $P_{\text{output}} = P_{\text{input}}/2$
- $V_{\text{out}}^2/R_1 = V_{\text{in}}^2/R_2$
- $R_1 = R_2$
- Transfer function  $|H|$  is the ratio between  $V_{\text{out}}$  and  $V_{\text{in}}$ .
  - Use algebra to solve for  $H$
  - Use  $H$  to solve for  $\omega RC$  and plug in to solve  $\Phi$

$$|H| = \frac{R_2}{R_1} \frac{1}{\sqrt{1 + (\omega R_2 C)^2}}, \quad \phi = 180^\circ - \arctan(\omega R_2 C)$$


$$|H| = \frac{V_o}{V_i}$$
$$|H|^2 = 1/2$$

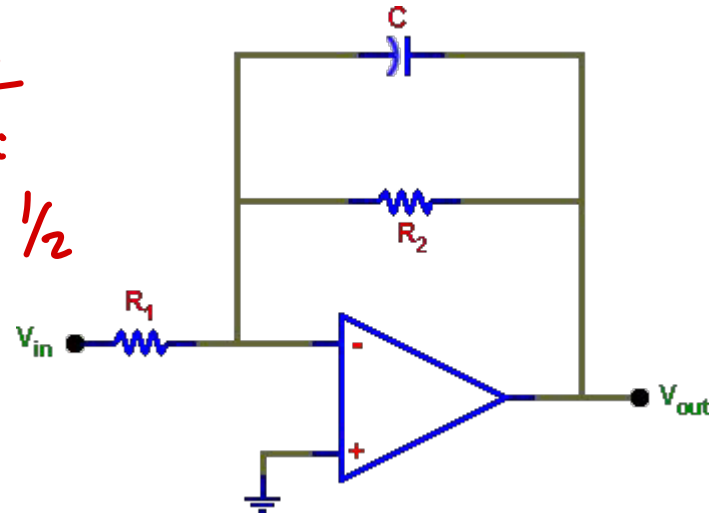

# Active Op Amp (inverting)


- DC input means no frequency.
- $\omega = 0$
- Solve for  $|H|$  and  $\Phi$

$$|H| = \frac{R_2}{R_1} \frac{1}{\sqrt{1 + (\omega R_2 C)^2}}, \quad \phi = 180^\circ - \arctan(\omega R_2 C)$$

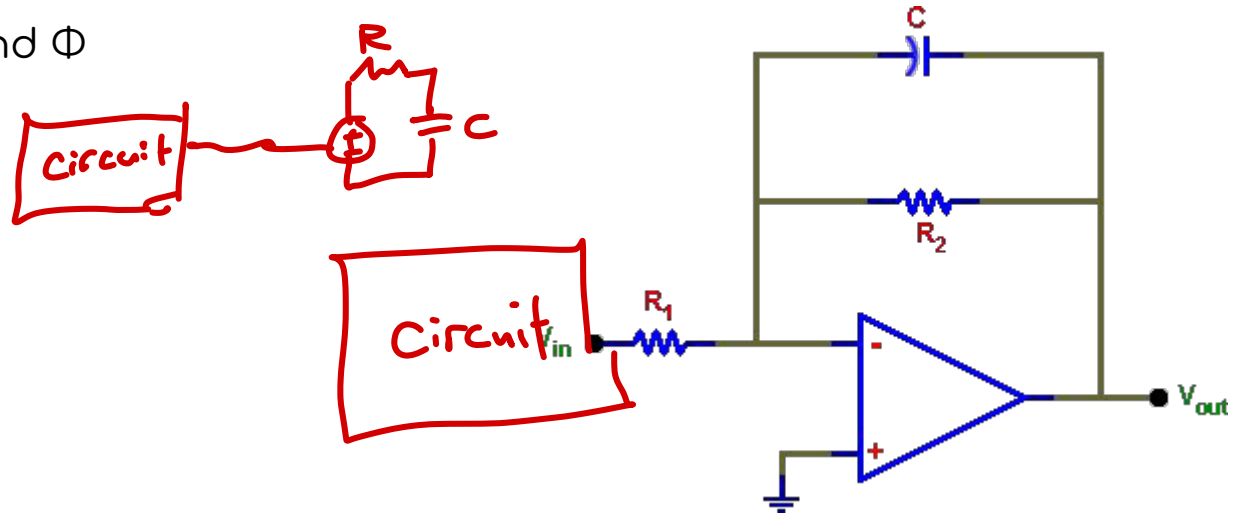
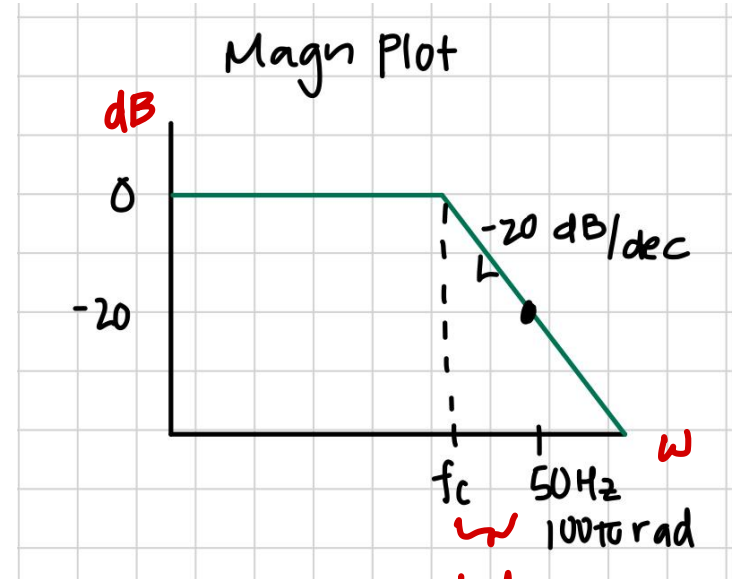
# Active Op Amp (inverting)

- Magnitude Plot for a Low Pass Filter
  - 20 Db are attenuated at 50 Hz.
  - Cut off frequency is at 0 dB.
  - Slope after cutoff is always -20DB per decade ( $10^1$ ) increase in frequency.
  - $10^1$  must have passed since cutoff frequency
- Solve for C
- R is V/I (given in problem)




$$f_c = \frac{1}{2RC\pi} = \frac{50}{10} = 5 \text{ Hz}$$
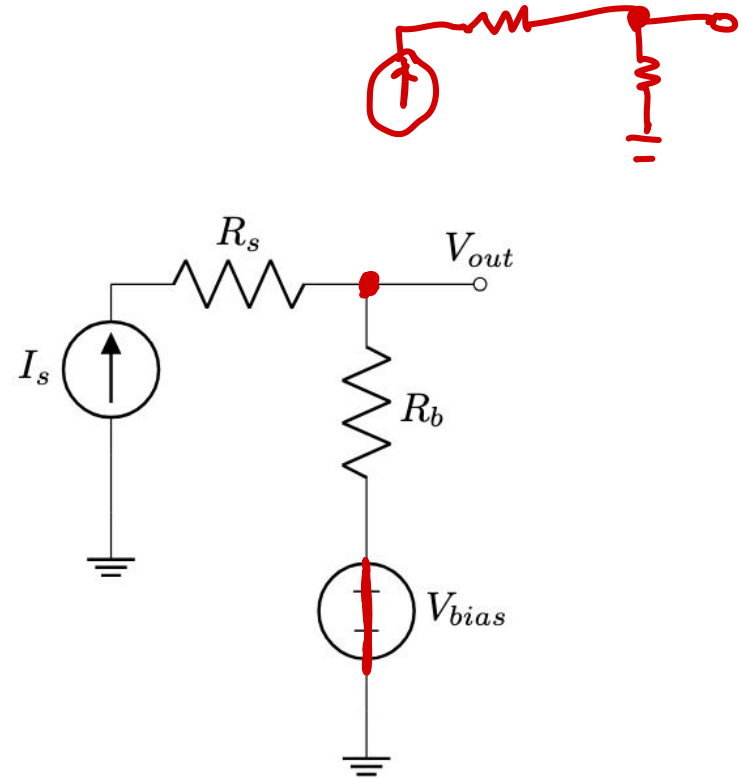
# Superposition


- Turn off current source, find  $V_{out,1}$ .
- Turn off voltage source, find  $V_{out,2}$ .
- $V_{out} = V_{out,1} + V_{out,2}$

$$\begin{matrix} \uparrow & \uparrow \\ V_{bias} & I_s R_b \end{matrix}$$


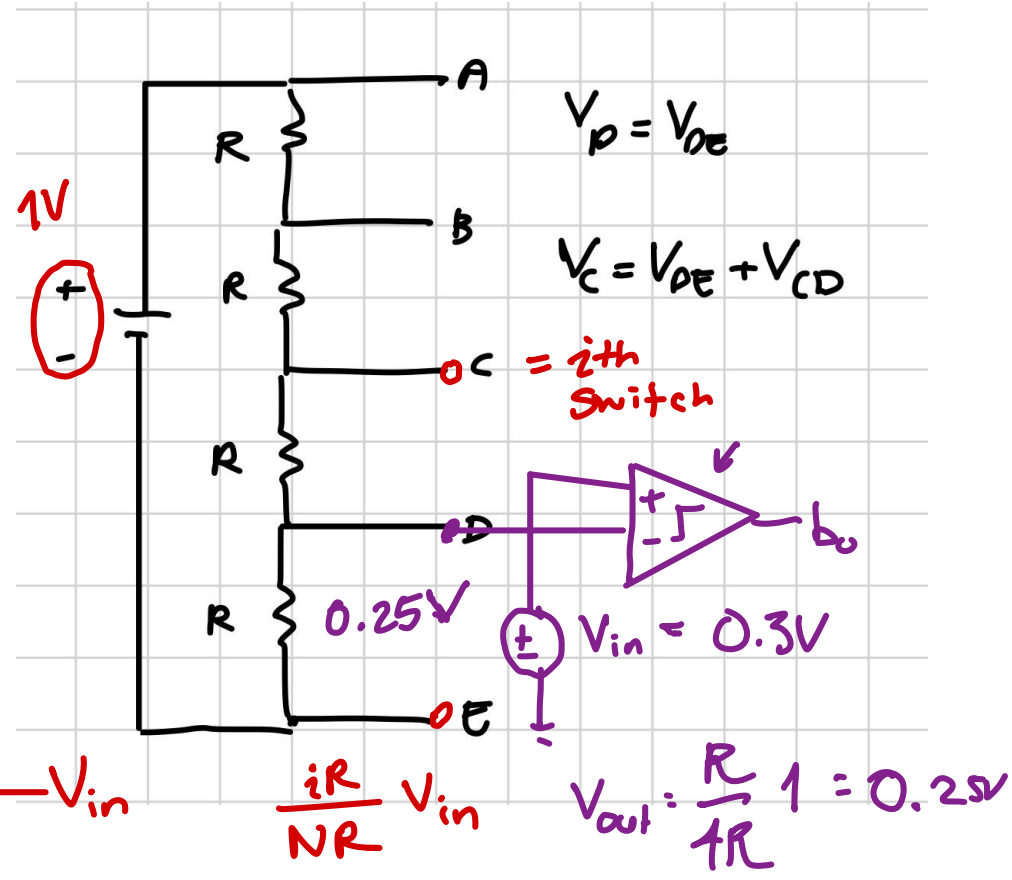
# Resistor Ladder

- Resistors split voltage into  $N$  equal parts (in this case,  $N=4$ ).
- If switch  $C$  is closed, voltage drop across  $CE$  gives  $V_{out}$
- Voltage drop  $CE$  = Voltage drop across  $DE + CD$
- Comparator outputs  $V_{DD}$  if voltage drop is less than  $0.3V$  and  $V_{SS}$  if not.



# Capacitor

- Use basic Q and I equations to get voltage derivative.
- Integrate both sides to get voltage in terms of current and initial voltage (init voltage is 0)
- Plug in values for I, V and t and solve for C (remember constants get taken out of integrals)

$$\boxed{I = \frac{dQ}{dt}} \quad \boxed{Q = CV} \quad \Rightarrow \quad \int \frac{dV}{dt} = \int \frac{1}{C} I(t)$$

$\frac{dQ}{dt} = C \frac{dV}{dt}$

$$v = \frac{1}{C} \int_0^T i \, dt + v_0$$

$$t = 1 \text{ hr}$$


$$i(t) = 5 \text{ nA}$$

$$V_{\text{out}} = 5 \text{ V}$$

$$V_0 = 0$$
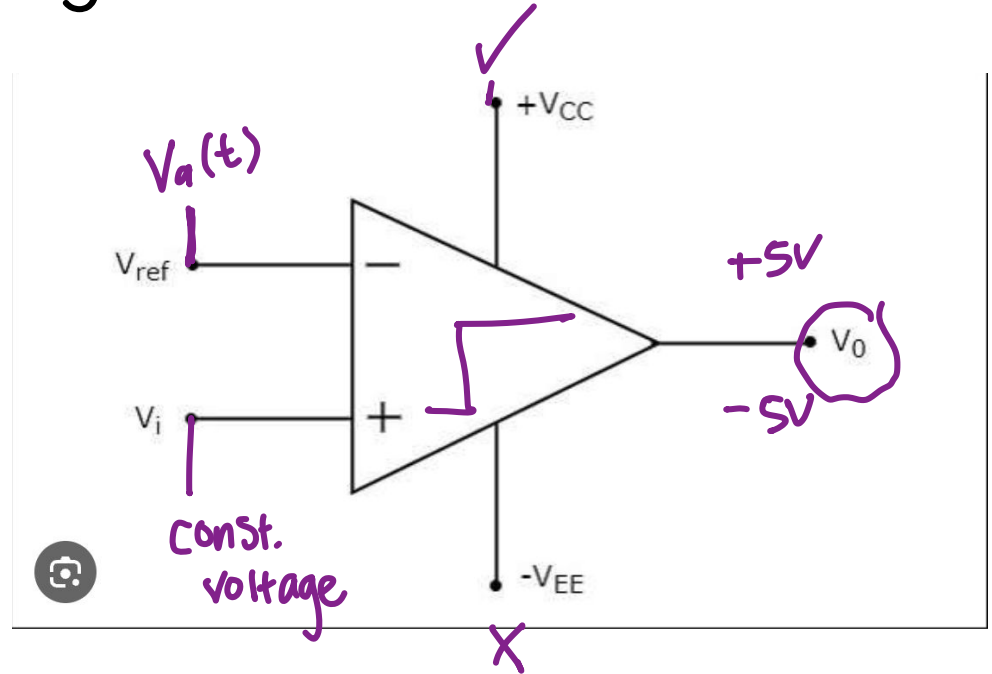
# Comparator Circuit Design

- $V_{CC}$  (output when reference is higher than input)
- $-V_{EE}$  (output when reference is lower than output)
- $V_i$  (input voltage you are comparing to reference, constant)
- What you have
  - Comparator
  - $V_o(t)$  - gives +5V after an hour of exposure
- What should you compare  $V_a$  to to ensure that the output switches from  $V_{EE}$  to  $V_{CC}$  when an hour of sunlight is reached?






# Shift + Scale Op Amp Circuit

- Goal: go from  $(-5V \rightarrow +5V)$  to  $(0V \rightarrow 5V)$
- This means halving  $V_{in}$  1  
 $(-2.5V \rightarrow 2.5V)$ , then adding 2.5  $(0V \rightarrow 5V)$  2
- Half  $V$  in with a gain of  $\frac{1}{2}$ .  
 Then use a summing amplifier to add 2.5 V


$$\left( \begin{array}{c} + \\ \triangleright \\ - \end{array} \right) V_o = 1 + \frac{R_2}{R_1} V_i$$
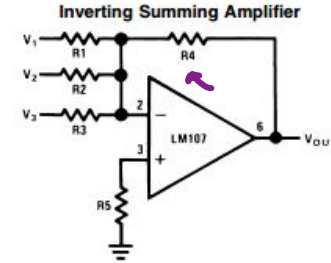
$$\left( \begin{array}{c} + \\ \triangleright \\ - \end{array} \right) V_o = -\frac{R_2}{R_1} V_i$$



$$V_{OUT} = -R4 \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

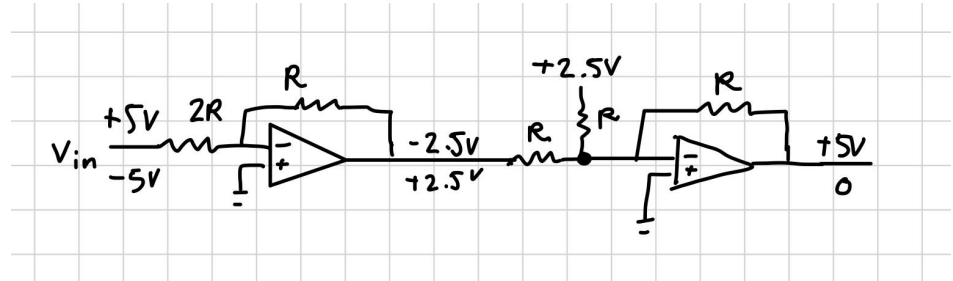$R5 = R1//R2//R3//R4$   
 For minimum offset error due to input bias current



- Stage 1 Gain =  $R/2R = \frac{1}{2}$ . Multiplies  $V$  in by  $-\frac{1}{2}$
- Stage 2 Adds 2.5 V with a summing junction and multiplies by -1 flipping voltage to  $0V \rightarrow +5V$ .